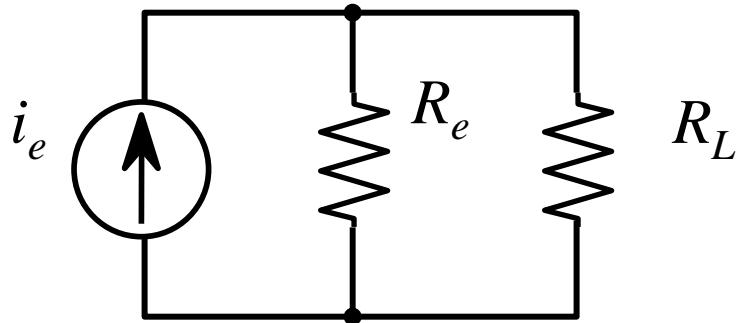


# Problem 1



Given


$$I_e = 10 \text{ mA}$$

$$R_e = 600 \Omega$$

$$R_L = 1.5 \text{ k}\Omega$$

Find the voltage across the load and the current through the load.

# Problem 1 Solution

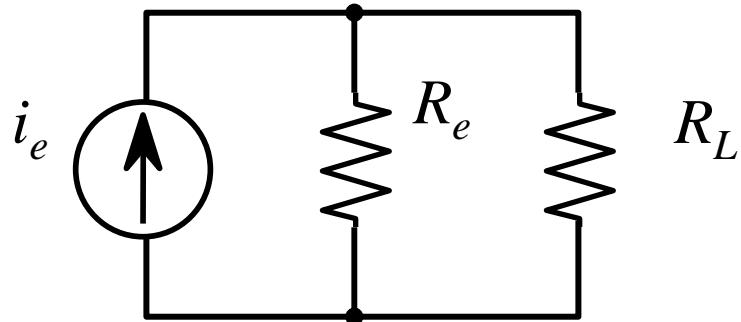

$$i_e = V_L \left( \frac{1}{R_e} + \frac{1}{R_L} \right)$$


$$i_L = \frac{V_L}{R_L}$$

```
Ie = 10e-3;  
Re = 600;  
RL = 1.5e3;  
Gp = 1/Re + 1/RL;  
VL = Ie/Gp;  
IL = VL/RL;  
fprintf('VL %.2f V, IL = %.2f mA\n',VL,IL*1e3);  
% test final formula  
fprintf('(alt) IL = %.2f mA\n',Re*Ie/(Re+RL)*1e3);
```

$$i_L = \frac{R_e}{R_L + R_e} i_e$$

Answers:  $V_L = 4.29$  V,  $I_L = 2.86$  mA

# Problem 2

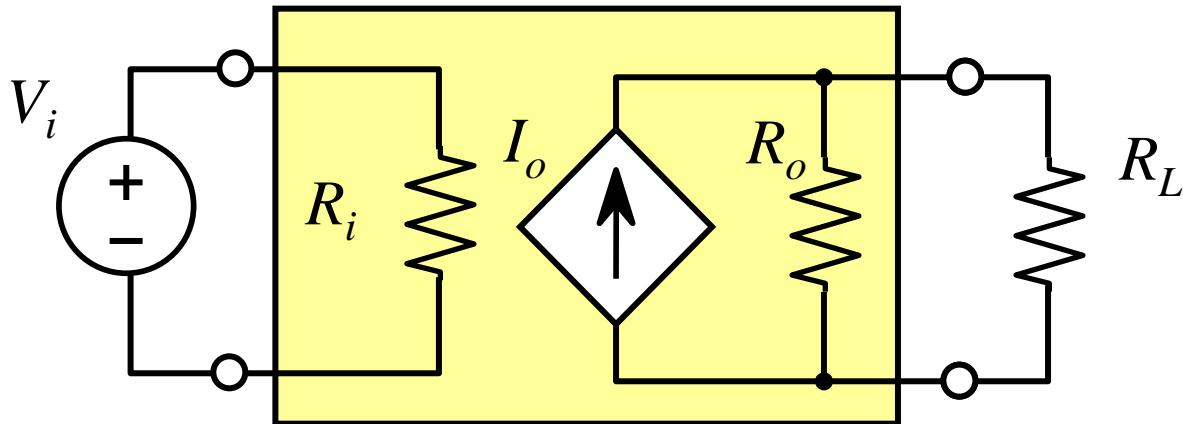

$$I_o = G_m V_i$$

Given

$$V_i = 0.1 \text{ V}$$

$$G_m = 100 \text{ mS}$$


$$R_i = 10 \text{ k}\Omega$$

$$R_o = 600 \Omega$$

$$R_L = 1.5 \text{ k}\Omega$$

Find the voltage across the load and the current through the load.  
Find the ratio of output power to input power.

# Problem 2 Solution

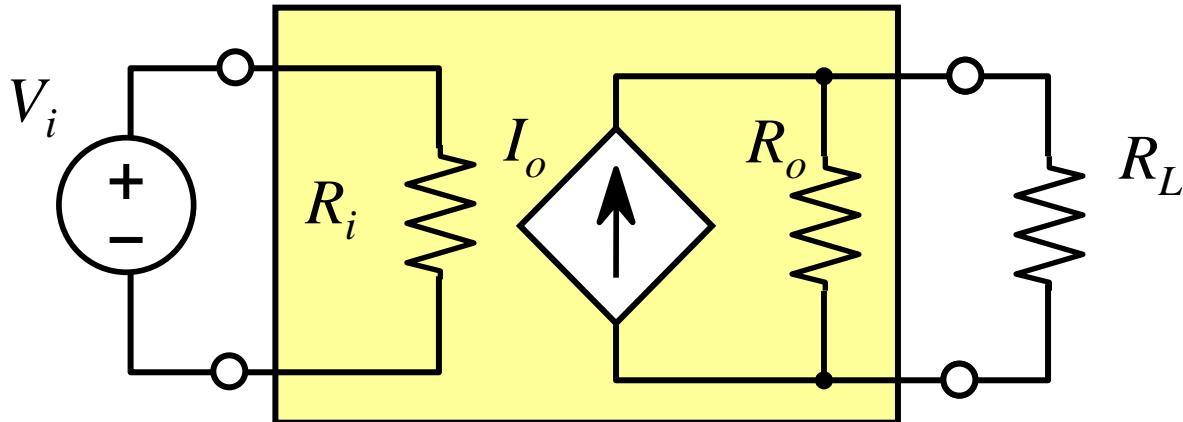

$$I_o = G_m V_i$$

$$I_o = G_m V_i = 10 \text{ mA}$$

Then its like the first problem.

Given

$$V_i = 0.1 \text{ V}$$

$$G_m = 100 \text{ mS}$$

$$R_i = 10 \text{ k}\Omega$$

$$R_o = 600 \Omega$$

$$R_L = 1.5 \text{ k}\Omega$$

$$P_L = I_L V_L = 2.86 \cdot 4.29 = 12.3 \text{ mW}$$

$$P_I = \frac{V_i^2}{R_i} = \frac{(0.1)^2}{10^4} = 10^{-8} \text{ W} = 10 \text{ nW}$$

$$\frac{P_L}{P_I} \approx 10^6$$

# Multisim Solution

