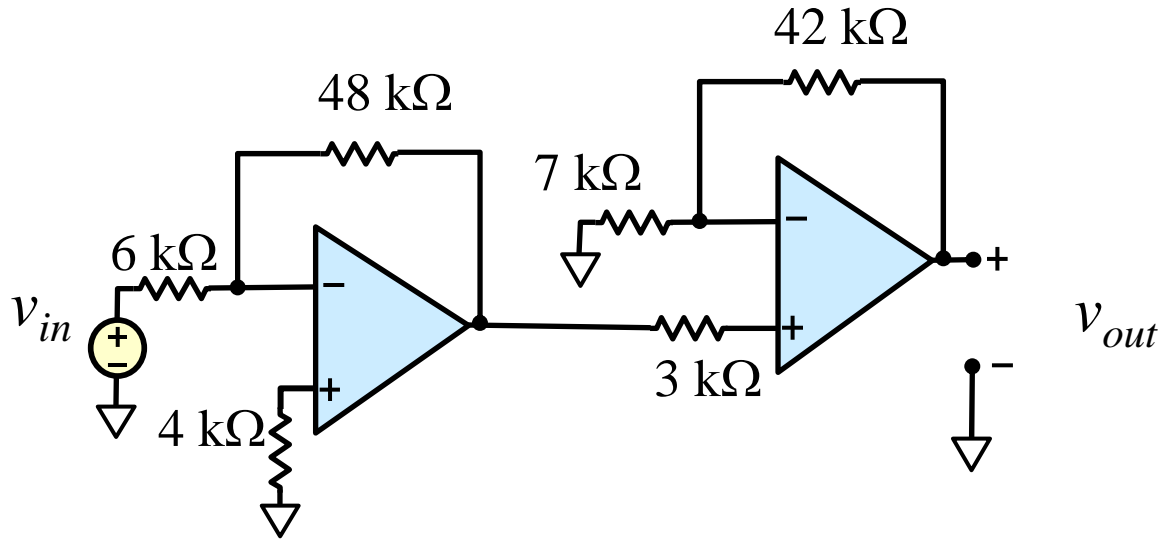



Example 1



Find the gain $\frac{v_{out}}{v_{in}}$

Find v_{out} if $v_{in} = 20 \text{ mV}$

Example 1 Solution

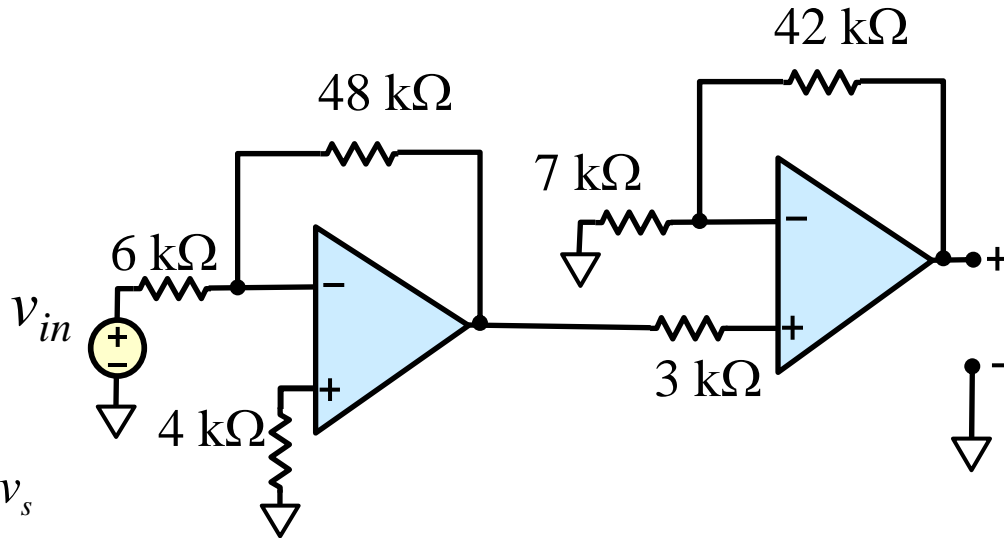

$$v_{out} = -\frac{R_f}{R_s} v_s$$

$$A_1 = -\frac{R_f}{R_s} = -8$$

$$A_2 = 1 + \frac{R_f}{R_s} = 7$$


v_{out}

$$v_{out} = \left[1 + \frac{R_f}{R_s} \right] v_s$$



$$\frac{v_{out}}{v_{in}} = A_2 A_1 = -56$$

$$v_{out} = -56 \cdot 20 \text{ mV} = -1.12 \text{ V}$$

Example 1 Multisim


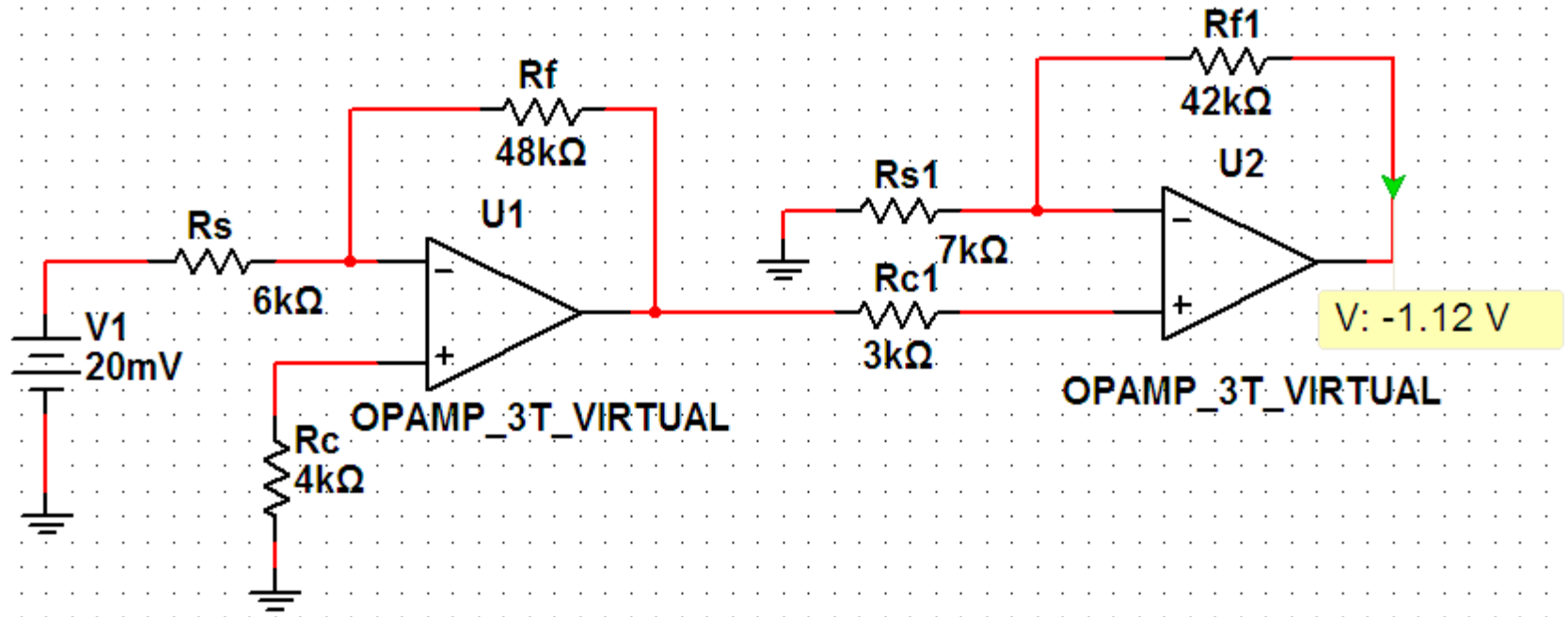


Example 2

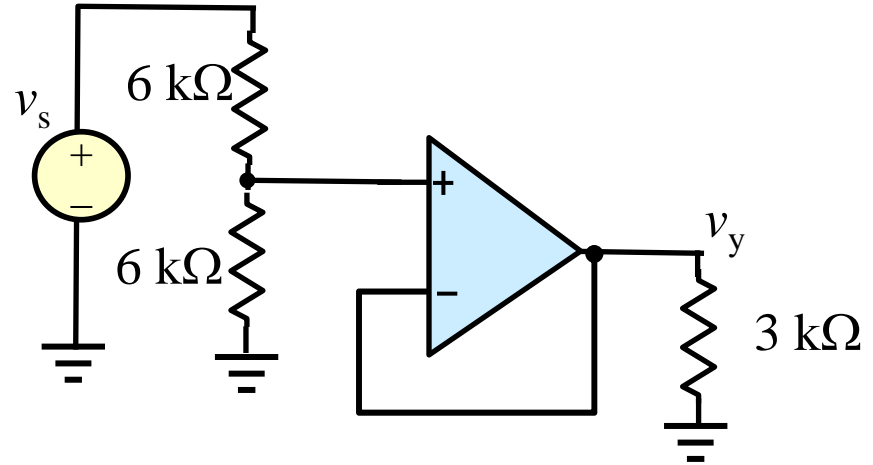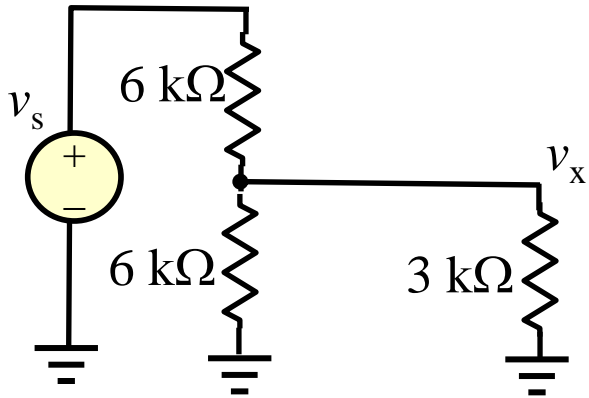

Find v_x (left diagram) and v_y (right diagram) if $v_s = 12\text{ V}$.

Example 2 Solution

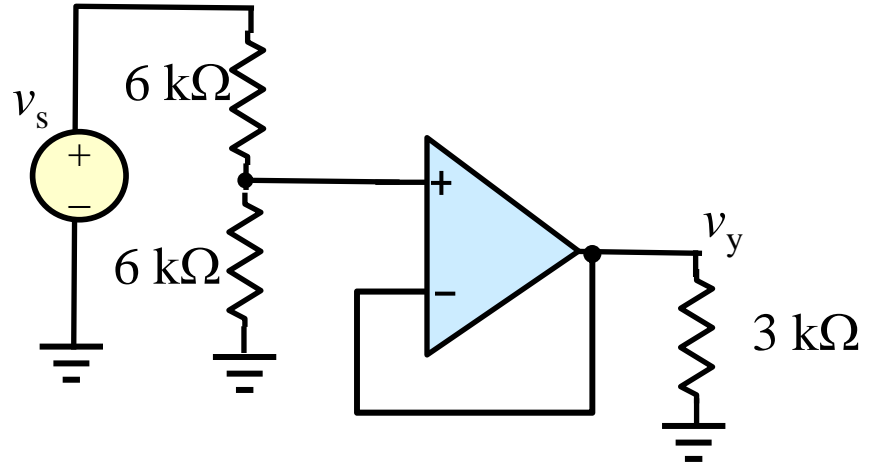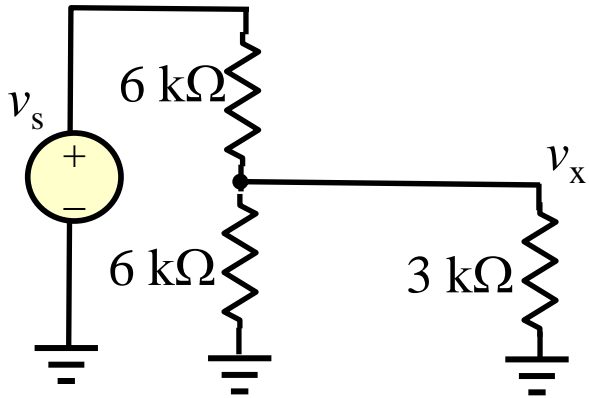

$$6\text{ k}\Omega \parallel 3\text{ k}\Omega = 2\text{ k}\Omega.$$

Output is voltage divider.


$$v_x = 3\text{ V}.$$

Opamp is voltage follower.


Input is voltage divider.

$$v_y = 6\text{ V}$$

Example 2 Multisim

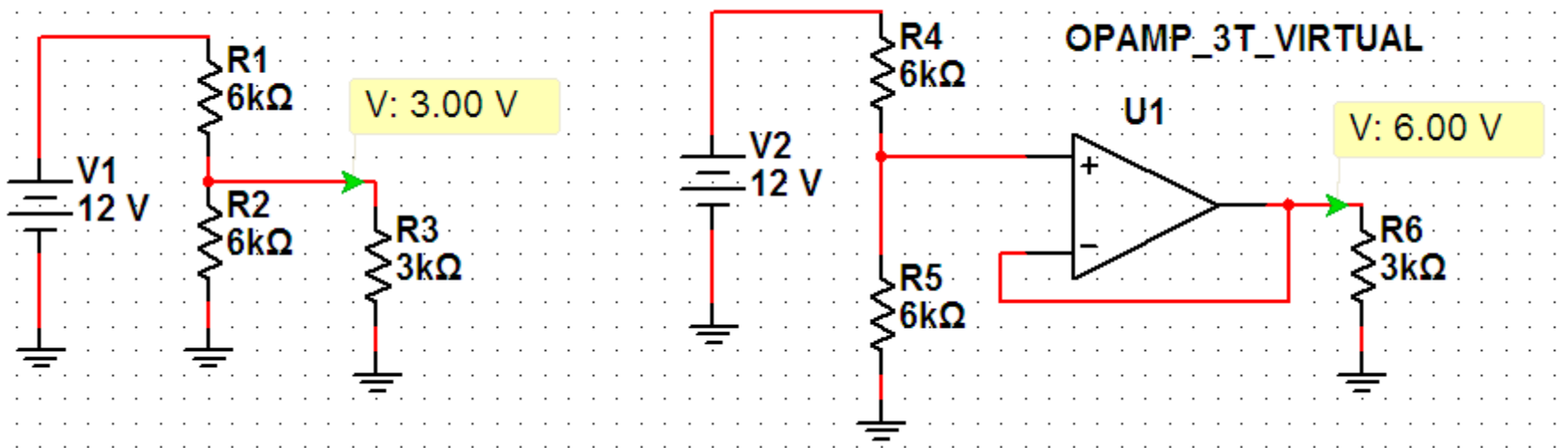

Example 3

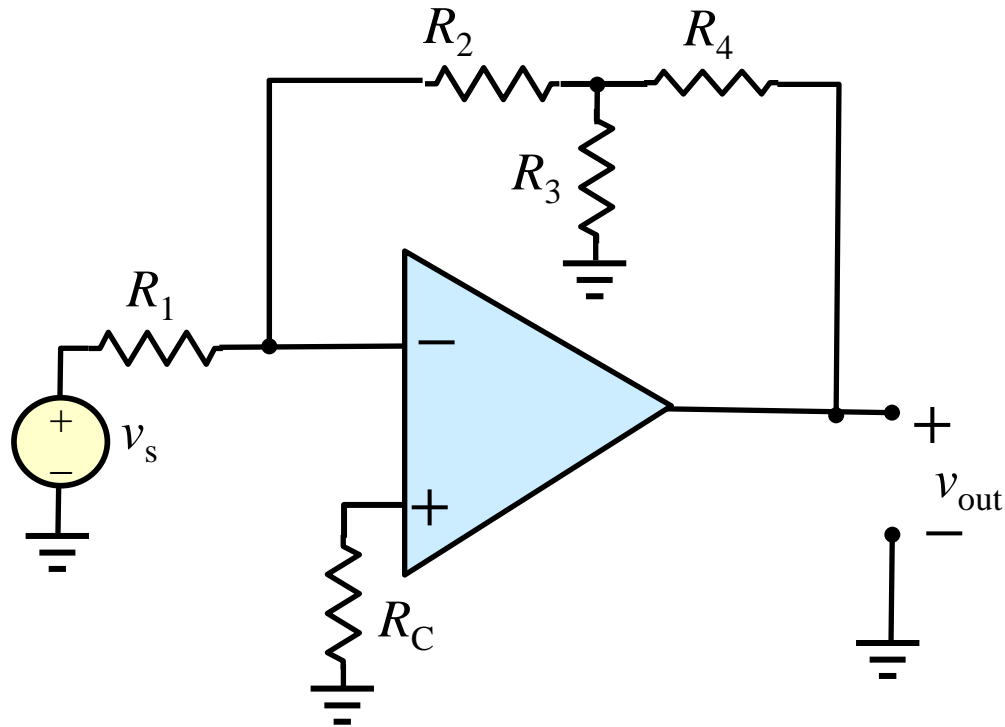

Find the voltage gain if $R_1 = R_3 = 1 \text{ k}\Omega$ and $R_2 = R_4 = 10 \text{ k}\Omega$.

Example 3 Solution (Analytic)

$$i_1 + i_2 = 0$$


$$i_4 - i_2 - i_3 = 0$$

$$\frac{v_s}{R_1} + \frac{v_x}{R_2} = 0$$

$$\frac{v_{out} - v_x}{R_4} - \frac{v_x}{R_2} - \frac{v_x}{R_3} = 0$$

$$\frac{v_s}{R_1} + \frac{v_x}{R_2} = 0$$
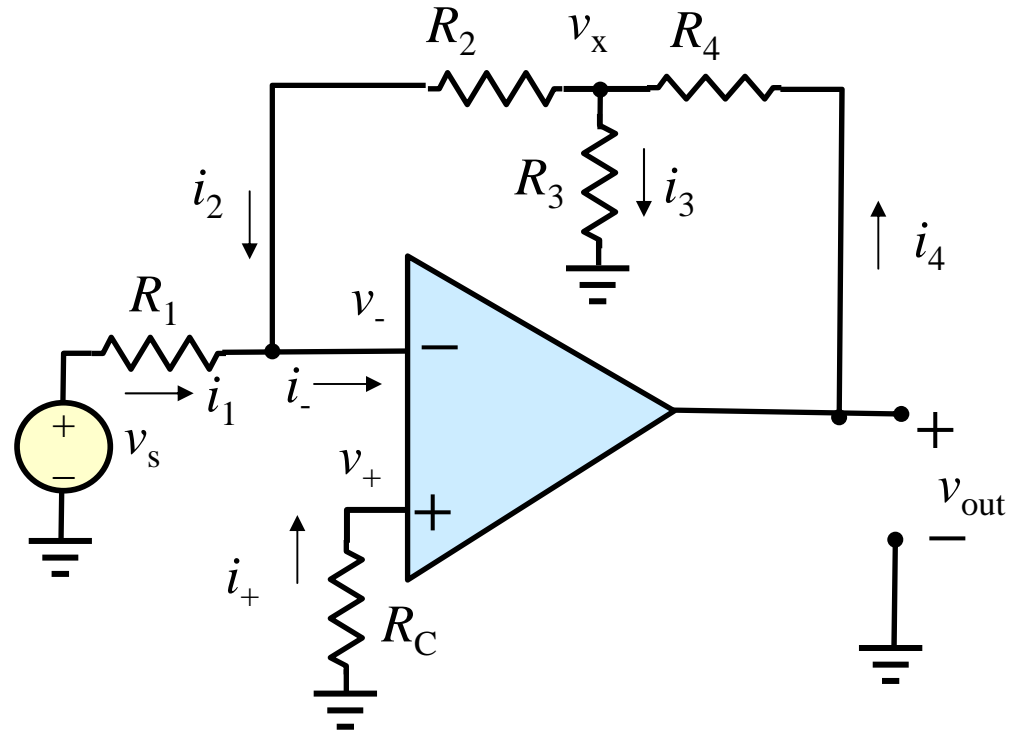
$$\frac{v_{out}}{R_4} - v_x \left(\frac{1}{R_4} + \frac{1}{R_2} + \frac{1}{R_3} \right) = 0$$



$$v_x = -\frac{R_2}{R_1} v_s$$

$$v_{out} = v_x \frac{R_4}{R_p}$$

$$v_{out} = -v_s \frac{R_2}{R_1} \frac{R_4}{R_p}$$


Example 3 Solution (Numeric)

$$v_{out} = -v_x \frac{R_2}{R_1} \frac{R_4}{R_p}$$

$$\frac{1}{R_p} = \frac{1}{R_4} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{10} + \frac{1}{10} + \frac{1}{1} = \frac{12}{10}$$
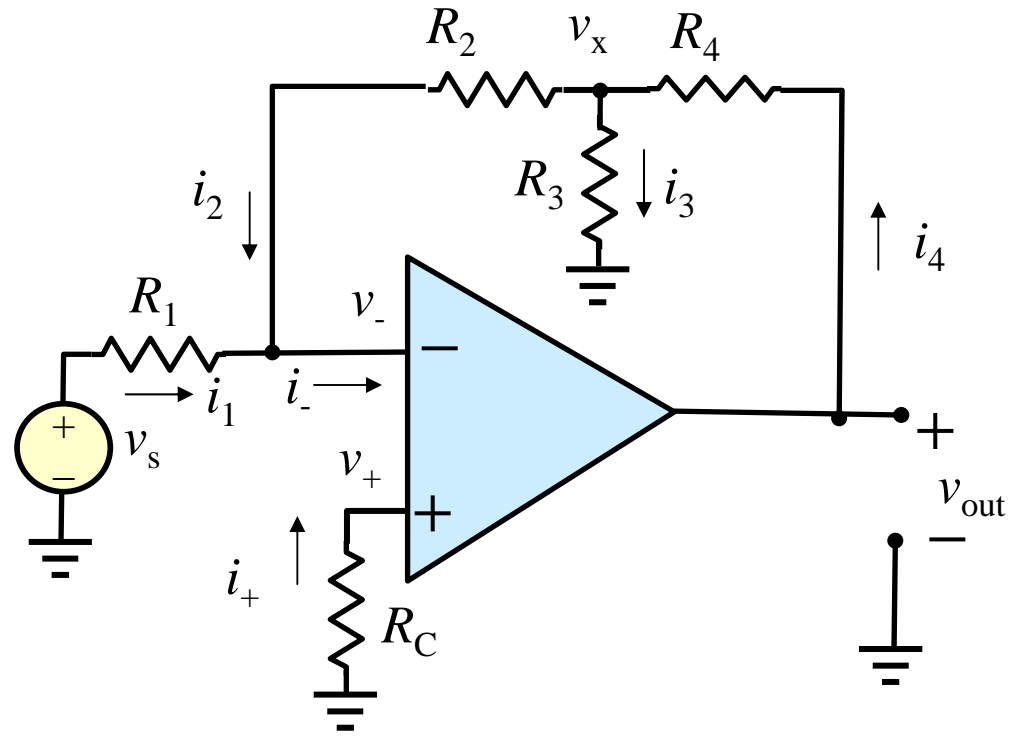
$$A = -\frac{R_2}{R_1} \frac{R_4}{R_p} = -\frac{10}{1} \cdot 10 \cdot \frac{12}{10} = -120$$



Example 3 Multisim

